

COEN 6501 Project Fall 2021 Specification

Jun Huang, Dawei Zuo, Yuelin Yao, and Xuesi Feng

Department of Electrical and Computer Engineering, Concordia University

COEN 6501: Digital Design and Synthesis

Dr. Marwan Ammar

December 6th, 2021

Table of Contents

Introduction	6
Heading II	6
Heading III	6
Project Requirement	7
Heading II	7
Heading III	7
Carry Select Adder	8
Full Adder	8
Two to one multiplexer	9
4-bit Ripple Carry Adder	10
4-bit Carry Select Adder	11
16-bit Carry Select Adder	13
24-bit Carry Select Adder	14
24-bit CSA Incrementor	15
Multiplication in Three Operands	16
Radix-4 Booth Algorithm Logic in Details	16
Example in Signed Number Multiplication	16
Example in Unsigned Number Multiplication	17
8-bit Radix-4 Booth Multiplier Circuit Implementation	18
Overall Circuit Design and RTL Description	18
Blocks Design	18
8-bit Triple Operands Multiplier Circuit Implementation	22
16-bit Triple Operands Multiplier Circuit Implementation	24
Overflow Handling	25
Heading II	25
Heading III	25
End Flag Generator	26

Non-pipelining Implementation	27
Heading II	27
Heading III	27
Pipelining Implementation	28
Heading II	28
Heading III	28
Synthesis and Analysis of the Arithmetic Circuit	29
Heading II	29
Heading III	29
References	30

List of Figures

1	Synthesized RTL Diagram of Full Adder Block	9
2	Simulation Wave Diagram of Full Adder Block	9
3	Synthesized RTL Diagram of 2-to-1 Multiplexer Block	10
4	Simulation Wave Diagram of 2-to-1 Multiplexer Block	10
5	Synthesized RTL Diagram of 4-bit Ripple Carry Adder Block	11
6	Simulation Wave Diagram of 4-bit Ripple Carry Adder Block	11
7	Synthesized RTL Diagram of 4-bit Carry Select Adder Block	12
8	Simulation Wave Diagram of 4-bit Carry Select Adder Block	13
9	Synthesized RTL Diagram of 16-bit Carry Select Adder Block	13
10	Simulation Wave Diagram of 16-bit Carry Select Adder Block	14
11	Synthesized RTL Diagram of 24-bit Carry Select Adder Block	14
12	Simulation Wave Diagram of 24-bit Carry Select Adder Block	15
13	Synthesized RTL Diagram of 24-bit Incrementor Block	15
14	Simulation Wave Diagram of 24-bit Incrementor Block	15
15	The Decoded Code Blocks of the Signed Multiplier	17
16	Process of the Algorithm for Signed Number	17
17	The Decoded Code Blocks of the Unsigned Multiplier	18
18	Process of the Slgorithm for Unisgned Number	18
19	Synthesized RTL Diagram of 8-bit Radix-4 Booth Multiplier	19
20	Synthesized RTL Diagram of Complement Generator	19
21	Simulation Wave Diagram of Complement Generator	20
22	Synthesized RTL Diagram of Booth Stage 0 Block	20
23	Simulation Wave Diagram of Booth Stage 0 Block	21
24	Synthesized RTL Diagram of Booth Stage 1 Block	21
25	Simulation Wave Diagram of Booth Stage 1 Block	22
26	Synthesized RTL Diagram of Triple 8-bit Operands Multiplier Circuit	23
27	Simulation Wave Diagram of Triple 8-bit Operands Multiplier Circuit	23
28	Synthesized RTL Diagram of Triple 16-bit Operands Multiplier Circuit	24
29	Simulation Wave Diagram of Triple 16-bit Operands Multiplier Circuit	24
30	ASMD Chart of the FSM of Different End Flag Generator	26
31	Synthesized RTL Diagram of 16-bit Radix-4 Booth Multiplier	31

List of Tables

1	Full Adder Truth Table	8
2	2-to-1 Multiplexer Truth Table	10
3	Code Table of Radix-4 Booth Algorithm	16

Introduction

Cervantes Saavedra, Raffel, and Wilson (1999) En un lugar de la Mancha, de cuyo nombre no quiero acordarme, no ha mucho tiempo que vivía un hidalgo de los de lanza en astillero, adarga antigua, rocín flaco y galgo corredor.

Heading II

Una olla de algo más vaca que carnero, salpicón las más noches, duelos y quebrantos los sábados, lantejas los viernes, algún palomino de añadidura los domingos, consumían las tres partes de su hacienda.

Heading III

El resto della concluían sayo de velarte, calzas de velludo para las fiestas, con sus pantuflos de lo mismo, y los días de entresemana se honraba con su vellorí de lo más fino.

Heading IV. Tenía en su casa una ama que pasaba de los cuarenta, y una sobrina que no llegaba a los veinte, y un mozo de campo y plaza, que así ensillaba el rocín como tomaba la podadera. Frisaba la edad de nuestro hidalgo con los cincuenta años; era de complexión recia, seco de carnes, enjuto de rostro, gran madrugador y amigo de la caza.

Heading V. Quieren decir que tenía el sobrenombre de Quijada, o Quesada, que en esto hay alguna diferencia en los autores que deste caso escriben; aunque por conjeturas verosímiles se deja entender que se llamaba Quijana.

Project Requirement

Heading II

Heading III

Heading IV.

Heading V.

Carry Select Adder

During the implementation of a multiplier, adders are needed. Different adder choices can have different effects on the delay and area. The outputs of ripple carry adder rely on the output carry of lower levels, so the RCA has an extremely long output chain and path. A carry select adder has a pair of Ripple Carry Adder performing the addition of a chunk of the two operands and a multiplexer to select the correct sum and carry out from the two RCAs. Compared to RCA, the carry select adder is a more efficient parallel adder.

In carry select adder, both sum and carry outputs are calculated for two alternatives: the input carry C_{in} '0' and '1'. Once the input carry is loaded, the correct calculation is chosen by a multiplexer to produce the desired output. Instead of waiting for the carry to calculate the sum, the sum will be correctly output as soon as the input carry delivered. The time used to compute the sum is then reduced that results in a good improvement in speed. Also, it can be formed into higher bit adders by cascading. So that extending the algorithm will be easier with the usage of CSAs.

The following will introduce the structures of the desired carry select adders used in this project.

Full Adder

The full adder is the fundamental digital component of various arithmetic logic unit, the circuit, which is composed of **XOR** gate, **AND** gate and **OR** gate, adds three inputs and produces two outputs. The full adder differs from the half adder in that the full adder has an input carry C_{in} , so that it can handle the carry in from the lower bit and output its carry out.

Multiple one-bit full adders can be cascaded to obtain a multi-bit full adder, which is used as a method to design subsequent circuits. The full adder is more widely used due to the feature that it can perform the addition of three bits. But at the same time, it requires additional gates. As a result, its delay increases. The truth table for the full adder is shown in Table 1.

Table 1

Full Adder Truth Table

A	B	Carry _{in}	Carry _{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


The equation for the full adder is defined at Expression (1).

$$\begin{aligned} \text{Sum} &= A \oplus B \oplus C_{in} \\ C_{out} &= (A \bullet B) + (C_{in} \bullet (A \oplus B)) \end{aligned} \quad (1)$$

The circuit for the full adder is shown in Figure 1.

Figure 1

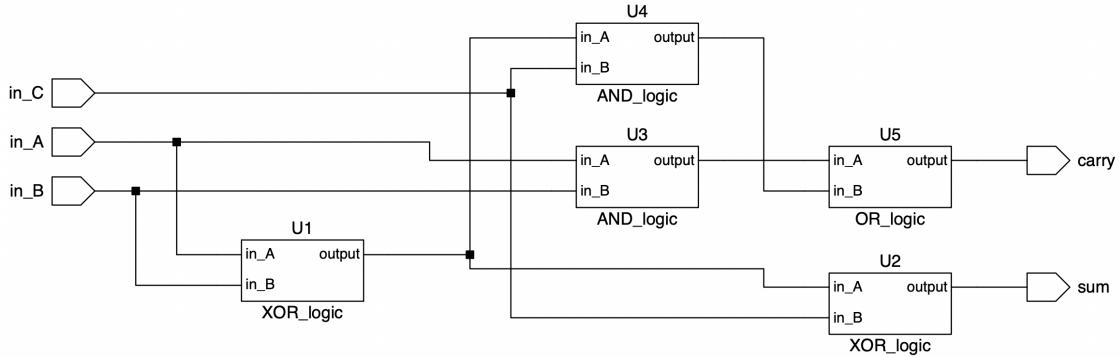
Synthesized RTL Diagram of Full Adder Block



The simulation results for the full adder are shown in Figure 2.

Figure 2

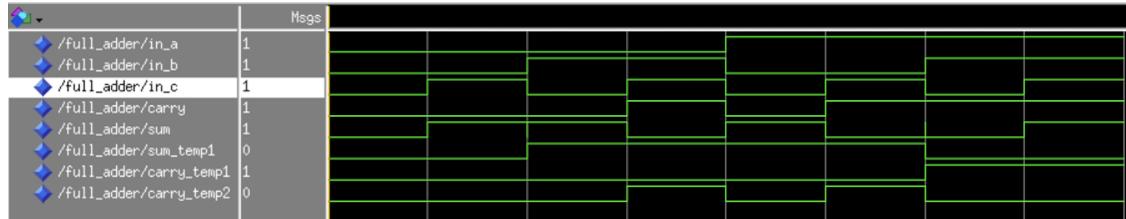Simulation Wave Diagram of Full Adder Block



Two to one multiplexer

The 2-to-1 multiplexer is a selector that has a switch to control the input, the circuit which consists of **AND** gate, **OR** gate and **NOT** gate. For a 2-to-1 multiplexer, the inputs are A and B , Sel is the select signal and Z is the output. Depending on the select signal, the output is connected to either of the inputs. If $Sel = 0$, then the output will be switched to input a , whereas if $Sel = 1$, then the output will be switched to input b . The truth table is shown in Table 2.

The equation for the multiplexer is defined at Expression (2)

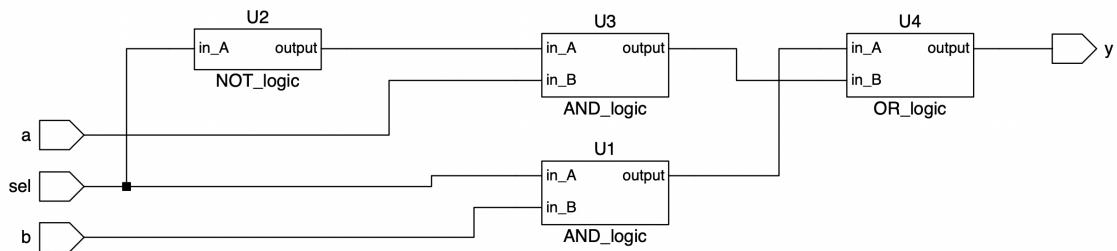
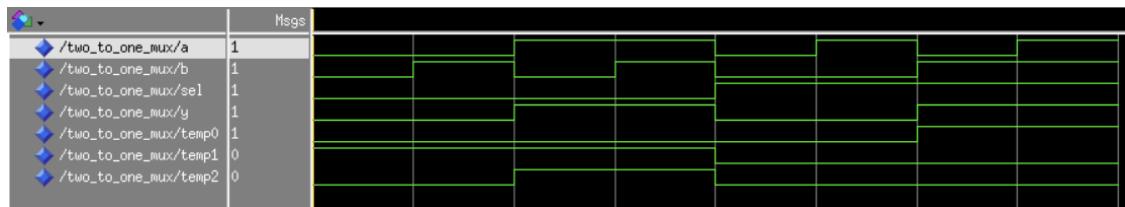
$$Y = (\overline{Sel} \bullet A) + (Sel \bullet B) \quad (2)$$

Table 2*2-to-1 Multiplexer Truth Table*

A	B	Select	Output
0	-	0	0
1	-	0	1
-	0	1	0
-	1	1	1

The circuit for the multiplexer is shown in Figure 3.

The simulation results for the multiplexer are shown in Figure 4.


Figure 3*Synthesized RTL Diagram of 2-to-1 Multiplexer Block***Figure 4***Simulation Wave Diagram of 2-to-1 Multiplexer Block*

4-bit Ripple Carry Adder

In order to build n-bit carry select adders which are suitable for this project, a 4-bit ripple carry adder block is the basic component. A ripple carry adder is cascaded in parallel by multiple full adder circuits, in which the carry out of each full adder is the carry in of the succeeding next most significant full adder. Four full adders are tied together to build the 4-bit ripple carry adder block for this project. Where A and B are 4-bit inputs, sum is the addition output of A and B , $Carry_{out}$ is the output carry which depends on C_{in} , C_1 , C_2 , C_3 . The circuit for the 4-bit ripple carry adder block is shown in Figure 5.

Figure 5

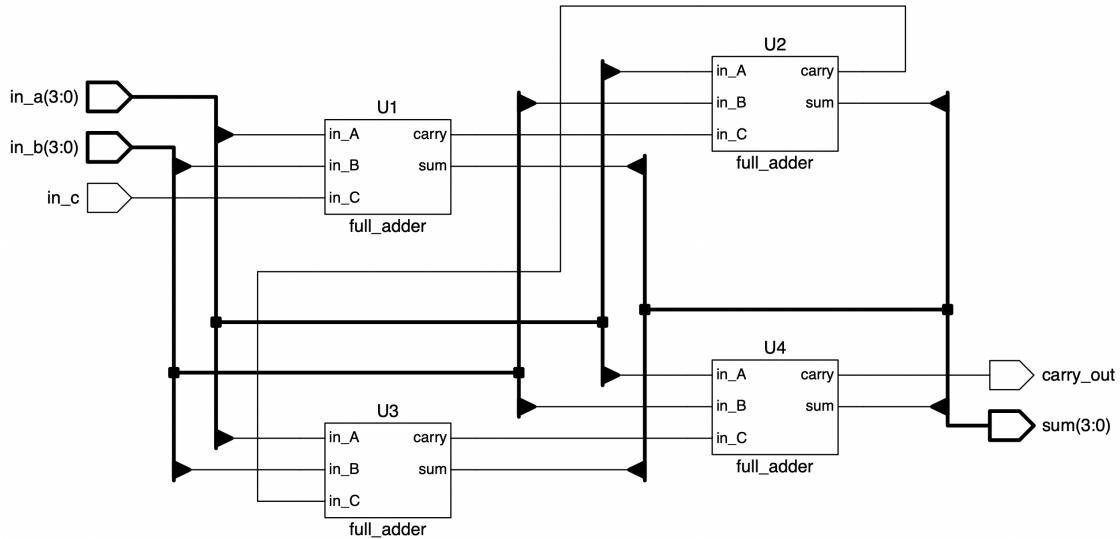Synthesized RTL Diagram of 4-bit Ripple Carry Adder Block




The selected simulation cases are shown below and the simulation results for the 4-bit ripple carry adder are shown in Figure 6.

- A general purpose test addition
- Overflow test
- Zeros test

Figure 6

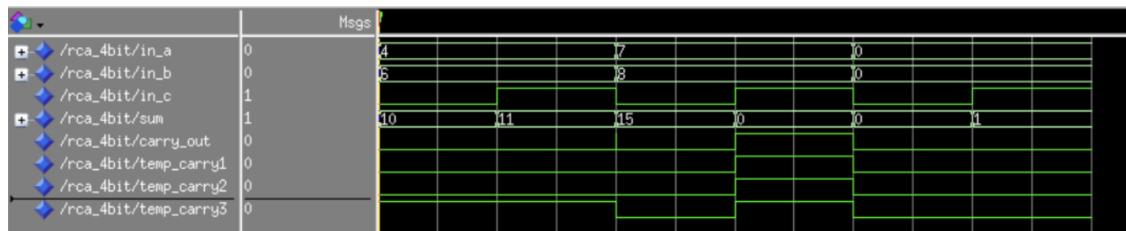Simulation Wave Diagram of 4-bit Ripple Carry Adder Block



4-bit Carry Select Adder

A basic building block size of carry select adder is four. A 4-bit carry select adder consists of two parallel 4-bit ripple carry adders and 2-to-1 multiplexers to perform the calculation twice. One of the 4-bit RCA block assumes that the input carry is 0 (RCA_0), the other assumes that the input carry is 1 (RCA_1). After the two results


are calculated, the correct sum, as well as the correct carry out, is then selected with the multiplexer once the correct carry in is known. The delay equation for the 4-bit carry select adder is defined below:

$$T_{CSA} = T_{mux} + 4 \times T_{full_adder} \quad (3)$$

The circuit for the 4-bit carry select adder is shown in Figure 7.

Figure 7

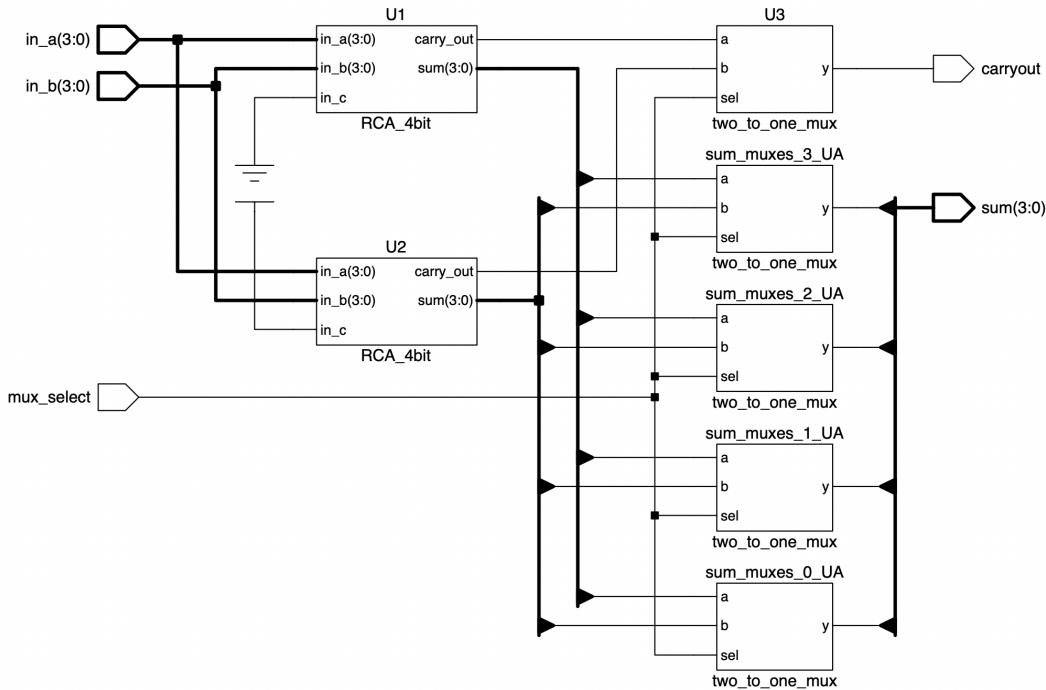Synthesized RTL Diagram of 4-bit Carry Select Adder Block




If the input carry C_{in} from the lower level is 0, the output carry of the RCA_0 is selected as the output carry of this 4-bit CSA block. If the input carry C_{in} from the lower level is 1, the output carry of the RCA_1 is selected as the output carry. At the same time C_{in} is used as the selection signal of 2-to-1 multiplexer to control whether the output of S3 to S0 comes from the RCA_0 or the RCA_1.

The simulation results for the 4-bit carry select adder are shown in Figure 8.

Figure 8

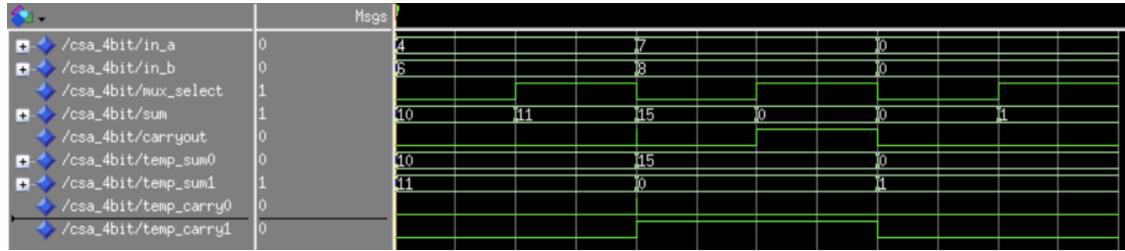Simulation Wave Diagram of 4-bit Carry Select Adder Block



16-bit Carry Select Adder


In this project, 16-bit carry select adder is used. A 16-bit carry select adder can be created using three 4-bit CSA blocks and one 4-bit RCA blocks. The first block is a 4-bit RCA, the inputs are two binary numbers from multiplier, so that there is no input carry and the C_{in} can be set to 0. Then the delay of this adder will be the delay of the four full adders, plus the delay of the three MUXs. The delay equation for the 16-bit carry select adder is defined below:

$$T_{CSA} = 3 \times T_{mux} + 4 \times T_{full_adder} \quad (4)$$

The circuit for the 16-bit carry select adder is shown in Figure 9.

Figure 9

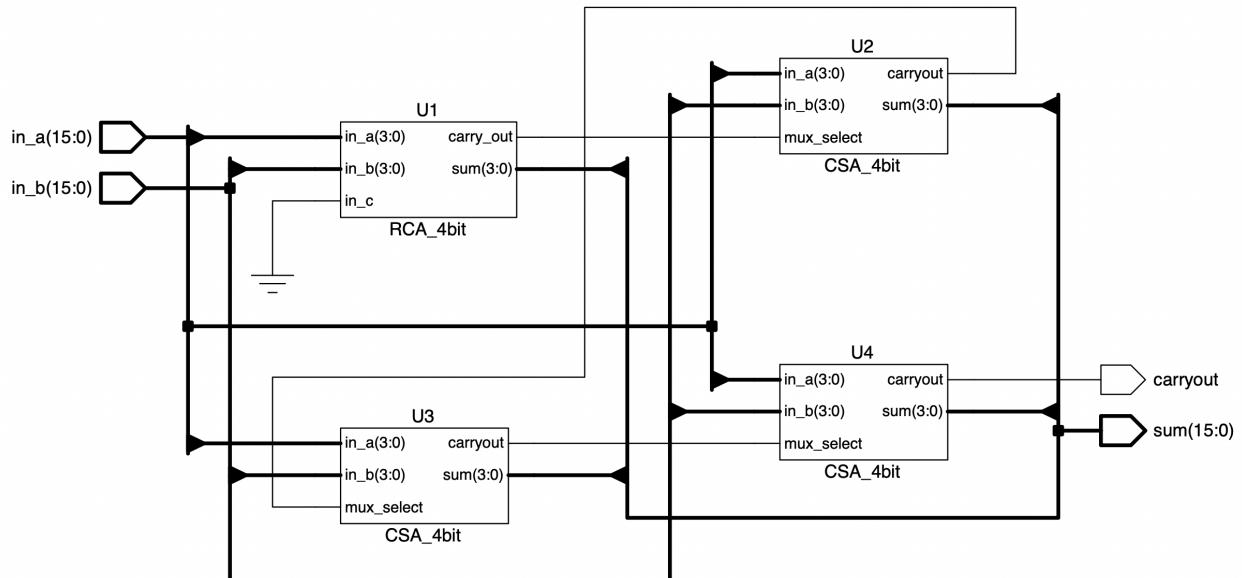Synthesized RTL Diagram of 16-bit Carry Select Adder Block



The simulation results for the 16-bit carry select adder are shown in Figure 10.

Figure 10

Simulation Wave Diagram of 16-bit Carry Select Adder Block



24-bit Carry Select Adder


Same principle as a 16-bit CSA, a 24-bit CSA is built up with five 4-bit CSA blocks and one 4-bit RCA block. Also, the first block is 4-bit RCA, the inputs are two binary numbers from multiplier, so that there is no input carry and the C_{in} can be set to 0. The delay equation for the 16-bit carry select adder is defined below:

$$T_{CSA} = 5 \times T_{mux} + 4 \times T_{full_adder} \quad (5)$$

The circuit for the 24-bit carry select adder is shown in Figure 9.

Figure 11

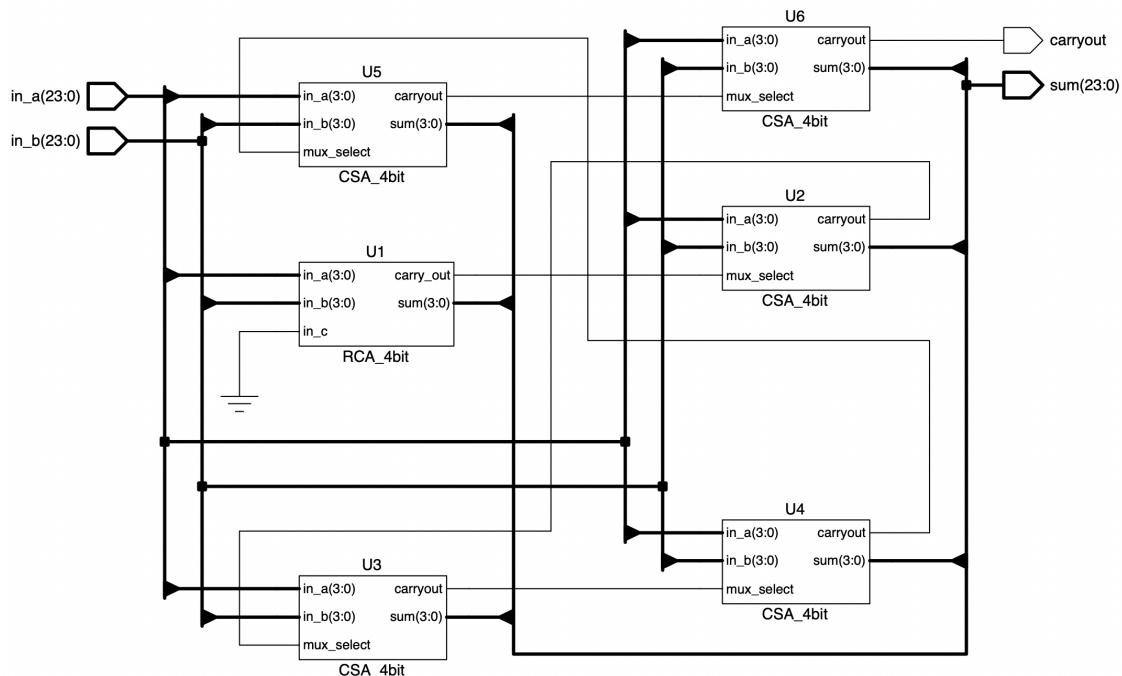
Synthesized RTL Diagram of 24-bit Carry Select Adder Block



The simulation results for the 24-bit carry select adder are shown in Figure 12.

Figure 12

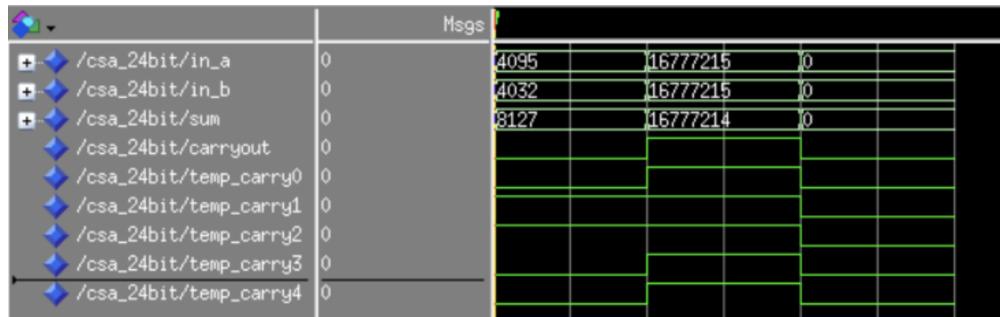Simulation Wave Diagram of 24-bit Carry Select Adder Block




24-bit CSA Incrementor

The incrementor used in this project were designed on the basis of the CSA. The principle is to define the input B of the CSA as a constant with the lowest bit of 1 and the rest of 0. Due to different bit requirements, a N-bit incrementor can be implemented by N-bit CSA. A 24-bit incrementor is used in this project. The circuit for the 24-bit incrementor is shown in Figure 13.

Figure 13

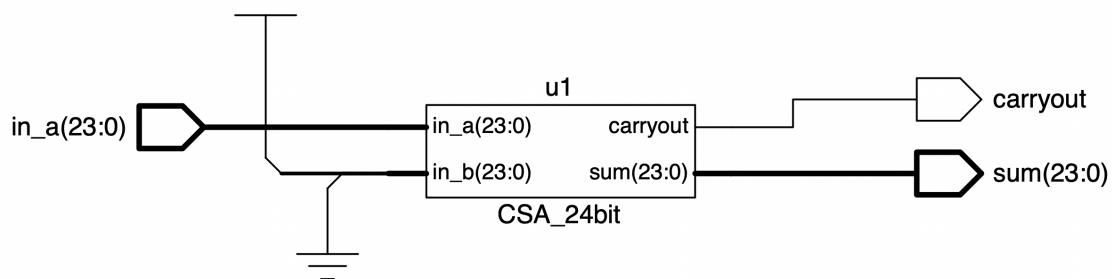Synthesized RTL Diagram of 24-bit Incrementor Block



The simulation results for the 24-bit incrementor are shown in Figure 14.

Figure 14

Simulation Wave Diagram of 24-bit Incrementor Block



Multiplication in Three Operands

The very first component of the ALU should be the circuit that calculating the result of $A^2 * B$. Hence the multiplication of two 8-bit operands circuit should be designed first, then the circuit for multiplying the product of the square A with the B should be designed later.

In general, the multiplication of two 8 bits operands in the shift-and-add algorithm or the radix-2 booth algorithm requires 8 steps of calculating eight partial products and then adding them together. By using the modified booth algorithm which is also known as radix-4 booth algorithm, the number of the partial products can be reduced to $2/n$ where n is the bit length of the operand.

Not only because it's faster, but also because it saves more area compared with the previous two algorithms. Hence the project chooses to implement the radix-4 booth algorithm as the multiplication component of the ALU.

There is an extra partial product the circuit should consider since the booth algorithm is design for the signed number. In this case, the implemented algorithm requires $2/n + 1$ partial product for unsigned number to reach the final answer. This will be discussed in the following sections.

Radix-4 Booth Algorithm Logic in Details

Booth algorithm calculates the partial product by examining the “Code Table” on the second operand, the multiplier. The table requires certain blocks of bits from the right side to the left side of the multiplier, and for each block, the table provides the partial product respectively. Radix-2 requires 2 bits while radix-4 requires 3 bits. This is how the radix-4 algorithm reduces the partial products to a half. In this manner, the overlaps will occur in the partial products, hence the algorithm will do subtraction according to the “Code Table”.

Example in Signed Number Multiplication

When the algorithm is used for calculating two 8-bit signed number *0b01010110* which is 86 in decimal, and *0b00100011* which is 35 in decimal, the multiplier will be decoded as Figure 15 is shown. Then all partial products can be derived from the code blocks and the “Code Table” which is presented in Table 3.


Table 3

Code Table of Radix-4 Booth Algorithm

Code Blocks	Partial Product
000/111	0
001/010	$1 * \text{multiplicand}$
011	$2 * \text{multiplicand}$
100	$-2 * \text{multiplicand}$
101/110	$-1 * \text{multiplicand}$

Figure 15

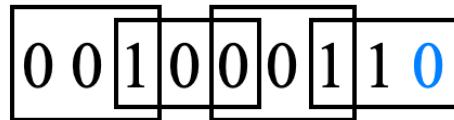The Decoded Code Blocks of the Signed Multiplier



Note. The blue bit is an extra bit which is added on the right of the LSB of the multiplier for completing the first code block.

The algorithm takes four blocks of code from the right to the left and retrieves the corresponding product with shifting two bits more than the previous product. Then perform the addition. The process of the algorithm is described in Figure 16.

Figure 16

Process of the Algorithm for Signed Number

110	1 1 1 1 1 1 1 1	1 0 1 0 1 0 1 0 1 0	partial product 1
001	0 0 0 0 0 0	1 0 1 0 1 1 0 0 0	partial product 2
100	1 1 1 1 0 1 0 1 0 1 0 0 0 0 0 0	0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	partial product 3
001	0 0 0 1 0 1 0 1 1 0	0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	partial product 4
	0 0 0 0 1 0 1 1 1 1 0 0 0 0 0 1 0		

Note. Bits in green color represent the product is extended to 16 bits. Bits in red color represent the shifted 2 bits leftward.


After the performance, the result $0b0000101111000010$ is 3010 in decimal which is the product of 86 and 35. As can be observed at the table, subtraction can be done by adding the negation of the number which is represented by 2's complement.

Example in Unsigned Number Multiplication

Applying the algorithm to unsigned operands is a little bit different. Because the MSB of the operand is treated as a valid number rather than the sign, the operands should extend to 9-bit by adding a “0” to the MSB. Hence an extra partial product will be added into the product. For instance, multiplicand $0b010010101$ which is 149 in decimal and multiplier $0b011001100$ which is 204 in decimal can be operated in the process as Figure 18 and Figure 18 are shown.

Figure 17

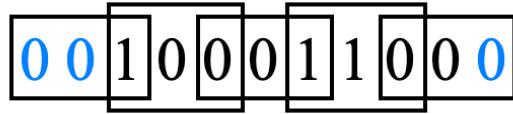The Decoded Code Blocks of the Unsigned Multiplier



Note. Two “0” are added to the MSB to complete the last code block. The second zero represent the sign bit of the operand which in this case will always be positive number.

Figure 18

Process of the Slgorithm for Unisgned Number

000	0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0	partial product 1
110	1 1 1 1 1 1 1 1 0 1 0 1 1 0 0 0	partial product 2
001	0 0 0 0 1 0 0 1 0 1 0 1 0 0 0 0	partial product 3
100	1 1 0 1 1 0 1 0 1 1 0 0 0 0 0 0	partial product 4
001	1 0 0 1 0 1 0 1 0 0 0 0 0 0 0 0	partial product 5
<hr/>		
	0 1 1 1 0 1 1 0 1 0 1 1 1 1 0 0	

Note. Bits in green color represent the product is extended to 16 bits. Bits in red color represent the shifted 2 bits leftward.

8-bit Radix-4 Booth Multiplier Circuit Implementation

Overall Circuit Design and RTL Description


As previous discussion, the booth multiplier component should contain the following blocks: 1. A 9-bit complementor for the negation of the multiplicand; 2. Five booth stage units for 5 partial products; 3. Four 16-bit adders for sum up the partial products. [Figure 19](#) presents the synthesized RTL diagram of the multiplier circuit.

The circuit will first calculates a 9-bit negation of operand multiplicand in 2’s complement. Then pass through all five booth stage blocks to get five 16-bit partial products. And finally sums those partial products up.

Blocks Design


This section will discuss the design of the complementor and five of the booth stages, the 16-bit CSA will be discussed in Section “Carry Select Adder”.

The 9-bit Complement Generator for the Negation of the Multiplier. Since the circuit uses negation addition to represent the subtraction, a complement generator should be introduced. The RTL diagram of the generator is shown in [Figure 20](#). The logic of the generator that uses a 2-to-1 mux is straightforward as Expression

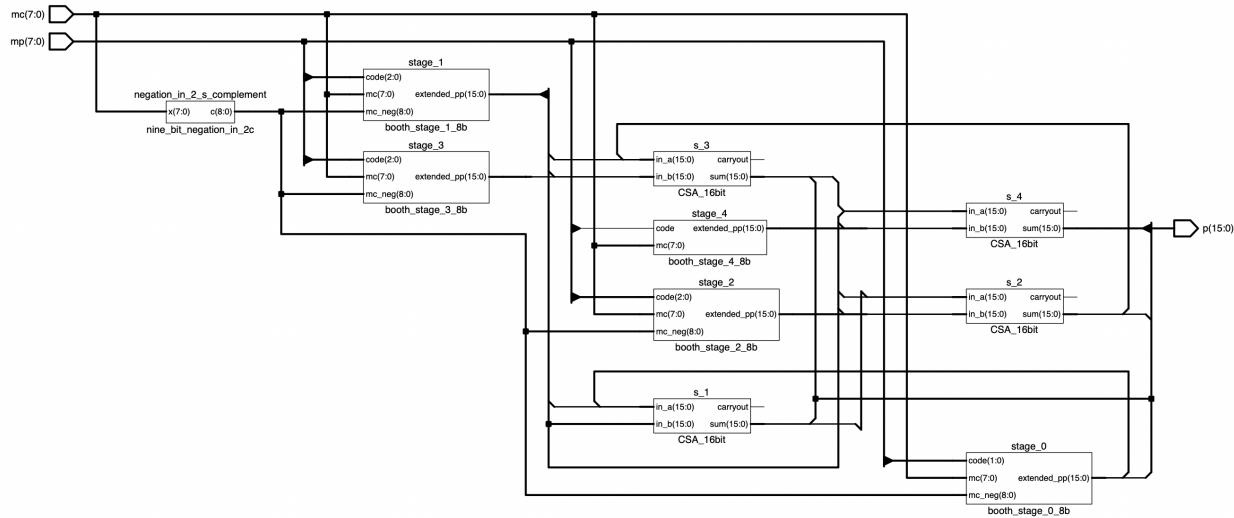Figure 19*Synthesized RTL Diagram of 8-bit Radix-4 Booth Multiplier*

(6) described. The simulation result is shown in Figure 21.

$$c = \begin{cases} concat(0, x), & \text{if } x = 00000000 \\ concat(1, (not x)) + 1, & \text{otherwise} \end{cases} \quad (6)$$

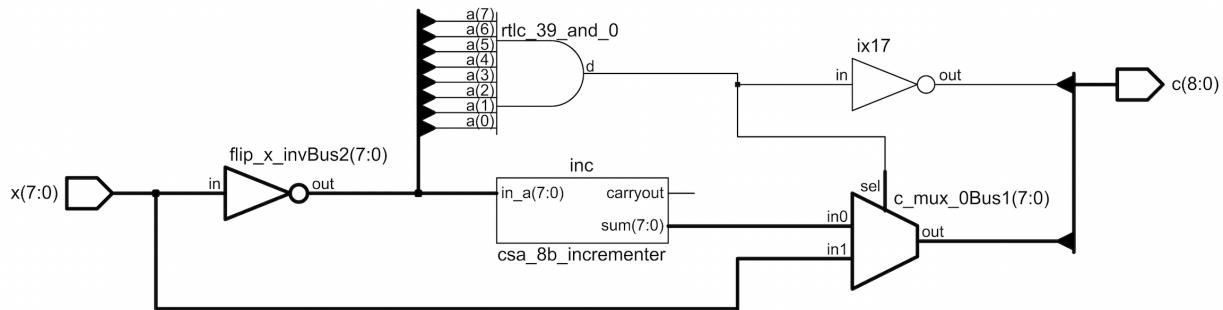Figure 20*Synthesized RTL Diagram of Complement Generator*

Booth Stage 0. Figure 22 and Expression (7) present the hardware implementation and the logic expression of the block. As the figure suggested, a booth stage block takes the 8-bit operand multiplicand and its 9-bit negation and two of the right most bits of the operand multiplier as input, and composes the 16-bit extended partial product as output by a 4-to-1 mux. The width of the *extended_sign_bits* will be 6. The simulation result is

Figure 21


Simulation Wave Diagram of Complement Generator

	Msgs		
/nine_bit_negation_in_2c/x	Data-	00000000	10110110
/nine_bit_negation_in_2c/c	Data-	00000000	101001010
/nine_bit_negation_in_2c/flip_x	Data-	11111111	01001001
/nine_bit_negation_in_2c/tmp	Data-	00000000	01001010

shown in Figure 23.

Figure 22

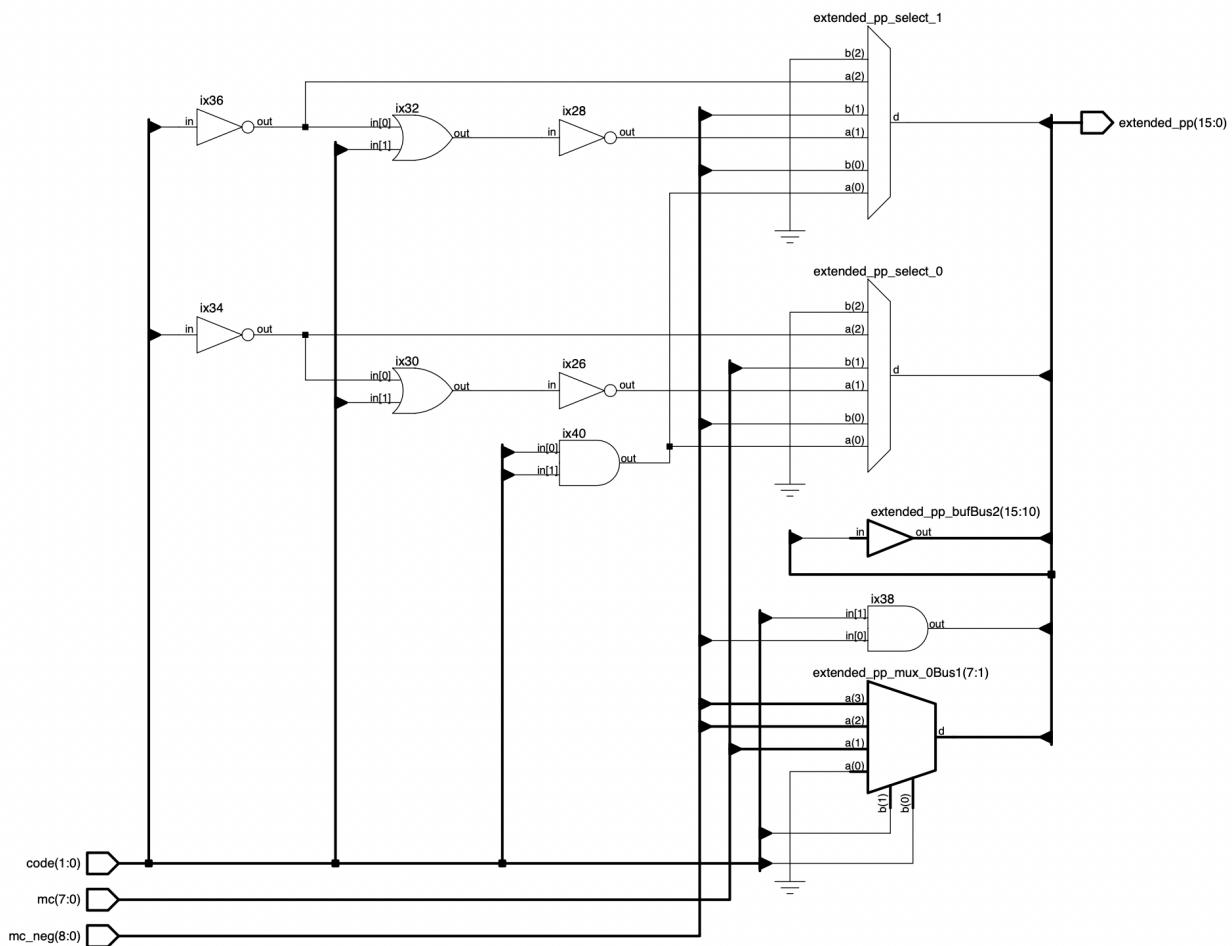Synthesized RTL Diagram of Booth Stage 0 Block



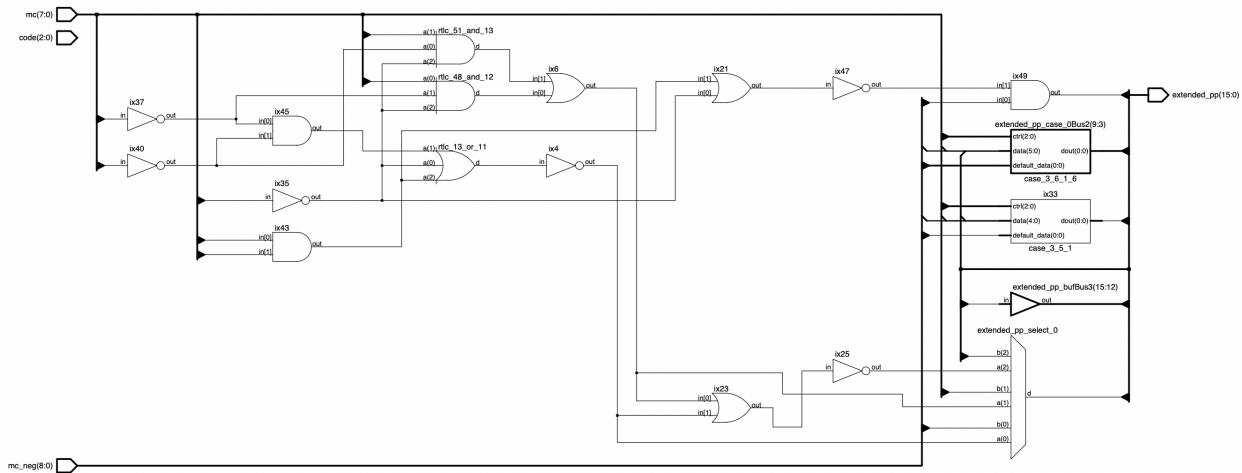
$$\begin{aligned}
partial_product = & \begin{cases} 0000000000, & \text{if } code = 00 \\ concat(00, mc), & \text{if } code = 01 \\ concat(mc_neg, 0), & \text{if } code = 10 \\ concat(mc_neg(8), mc_neg), & \text{else } code = others \end{cases} \\
extended_sign_bits = & (others \Rightarrow partial_product(9)) \\
extended_pp = & concat(extended_sign_bits, partial_product)
\end{aligned} \tag{7}$$

Figure 23*Simulation Wave Diagram of Booth Stage 0 Block*

Msgs	Data	Data	Data	Data
+ /booth_stage_0_8b/mc	00100110			
+ /booth_stage_0_8b/mc_neg	111011010			
+ /booth_stage_0_8b/code	00	01	10	11
+ /booth_stage_0_8b/partial_product	0000000000	0000100110	1110110100	1111011010
+ /booth_stage_0_8b/extended_sign_bits	000000		111111	
+ /booth_stage_0_8b/extended_pp	0000000000000000	0000000000100110	1111111110110100	1111111110110100

Note. Four code values were provided to simulate the *extended_pp*.

Booth Stage 1. Figure 24 and Expression (8) present the hardware implementation and the logic expression of the block. Different from booth stage 0 block, this stage takes 3 bits from the operand multiplier. With considering the right shift during the algorithm, the width of the *extended_sign_bits* will be 4, and “00” will be added to the end. The simulation result is shown in Figure 25.

Figure 24*Synthesized RTL Diagram of Booth Stage 1 Block*

$$\begin{aligned}
partial_product = & \begin{cases} 0000000000, & \text{if } code = 000|111 \\ concat(00, mc), & \text{if } code = 001|010 \\ concat(0, mc, 0), & \text{if } code = 011 \\ concat(mc_neg, 0), & \text{if } code = 100 \\ concat(mc_neg(8), mc_neg), & \text{else } code = others \end{cases} \\
extended_sign_bits &= (others \Rightarrow partial_product(9)) \\
extended_pp &= concat(extended_sign_bits, partial_product, 00)
\end{aligned} \tag{8}$$

Figure 25*Simulation Wave Diagram of Booth Stage 1 Block*

(a) With Code Values: 000/001/010/011

Msgs	Data	Data	Data	Data
/booth_stage_1_8b/mc	00100110			
/booth_stage_1_8b/mc_neg	111011010			
/booth_stage_1_8b/code	000	001	010	011
/booth_stage_1_8b/partial_product	0000000000	0000100110		0001001100
/booth_stage_1_8b/extended_sign_bits	0000			
/booth_stage_1_8b/extended_pp	0000000000000000	0000000010011000		0000000100110000

(b) With Code Values: 100/101/110/111

Msgs	Data	Data	Data	Data
/booth_stage_1_8b/mc	00100110			
/booth_stage_1_8b/mc_neg	111011010			
/booth_stage_1_8b/code	100	101	110	111
/booth_stage_1_8b/partial_product	1110110100	1111011010		0000000000
/booth_stage_1_8b/extended_sign_bits	1111			0000
/booth_stage_1_8b/extended_pp	1111111011010000	1111111101101000		0000000000000000

Note. Eight code values were provided to simulate the *extended_pp*.

Booth Stage 2, 3, and 4. Booth stage 2 and 3 blocks share the same idea of booth stage 1 except they shift more bit to the right. As for booth stage 4 block, it only takes the MSB from the operand multiplier. Expression (9) shows its logic.

$$extended_pp = \begin{cases} 0000000000000000, & \text{if } code = 0 \\ concat(mc, 00000000), & \text{else } code = others \end{cases} \tag{9}$$

8-bit Triple Operands Multiplier Circuit Implementation

Once the 16-bit product of A^2 which marked as *product_aa* is calculated, it will then multiply with the 8-bit input *B*. To perform multiplication with a 16-bit operand and a 8-bit operand, the circuit divides the 16-bit operand

into two 8-bit operands. This is to reuse the 8-bit multiplier block that is designed before.

The product of multiplying the higher 8-bit of *product_aa* and *B* will be marked as *product_haa_b*, and it will be extended to 24 bits by shifting 8 bits rightwards. The product of multiplying the lower 8-bit of *product_aa* and *B* will be marked as *product_laa_b*, and it will be extended to 24 bits by adding 8 zeros to its left. Then adds those two extended 24-bit number together will be the result of $A^2 * B$.

Figure 26 presents the RTL description of the circuit and Figure 27 presents the simulation result.

Expression (10) shows the arithmetic process of the $A^2 * B$.

$$\begin{aligned}
 aa &= a * a \\
 laa_b &= aa[7,0] * b \\
 haa_b &= aa[15,8] * b \\
 aab_m &= concat(haa_b, 00000000) \\
 aab_l &= concat(00000000, laa_b) \\
 p &= aab_m + aab_l
 \end{aligned} \tag{10}$$

Figure 26

Synthesized RTL Diagram of Triple 8-bit Operands Multiplier Circuit

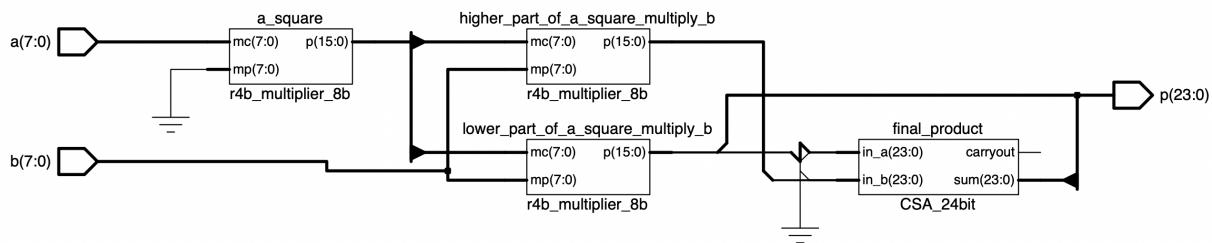


Figure 27

Simulation Wave Diagram of Triple 8-bit Operands Multiplier Circuit

	Msgs				
+ ⚡ /tri_multiplier_8b/a	0 0	178	0	210	255
+ ⚡ /tri_multiplier_8b/b	0 0	46	0	0	255
+ ⚡ /tri_multiplier_8b/product_aa	0 0	31684	0	44100	65025
+ ⚡ /tri_multiplier_8b/product_laa_b	0 0	9016	0	0	255
+ ⚡ /tri_multiplier_8b/product_haa_b	0 0	5658	0	0	64770
+ ⚡ /tri_multiplier_8b/product_aab_m	0 0	1448448	0	0	16581120
+ ⚡ /tri_multiplier_8b/product_aab_l	0 0	9016	0	0	255
+ ⚡ /tri_multiplier_8b/p	0 0	1457464	0	0	16581375

16-bit Triple Operands Multiplier Circuit Implementation

Like the 8-bit version, the 16-bit implementation of the booth multiplier will need 9 blocks of booth stage to calculate 9 partial products. Because of the characteristic of the algorithm, the 16-bit version can not reuse or extend from the 8-bit version circuit designed before. Hence the circuit will need to build every block from scratch. **This is one of the drawbacks of the booth algorithm: lack of expandability.**

Figure 28 presents the RTL description of the triple 16-bit operands multiplier circuit and Figure 29 presents the simulation result. Figure 31 presents the RTL description of the 16-bit booth multiplier circuit.

Figure 28

Synthesized RTL Diagram of Triple 16-bit Operands Multiplier Circuit

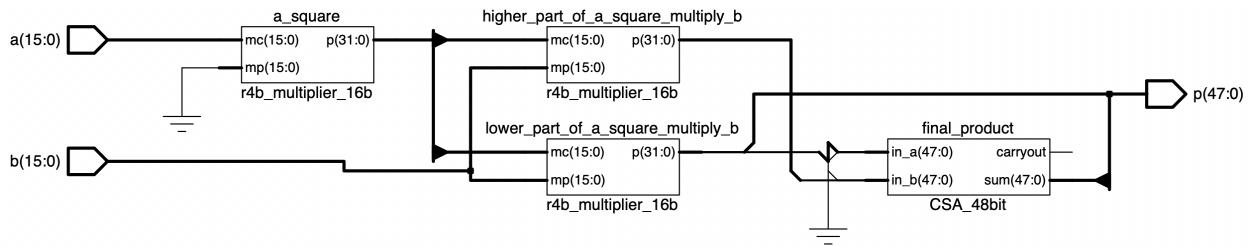


Figure 29

Simulation Wave Diagram of Triple 16-bit Operands Multiplier Circuit

	Msgs	Data-0	Data-1	Data-2	Data-3
+◆ /tri_multiplier_16b/a		36096	0	11507	65535
+◆ /tri_multiplier_16b/b		60624	0	0	65535
+◆ /tri_multiplier_16b/product_aa		1451457604	0	132411049	4294836225
+◆ /tri_multiplier_16b/product_haa_b		1928570688	0		65535
+◆ /tri_multiplier_16b/product_haa_b_m		1342639728	0		4294770690
+◆ /tri_multiplier_16b/product_aab_m		67991237214208	0		281462091939840
+◆ /tri_multiplier_16b/product_aab_l		1928570688	0		65535
+◆ /tri_multiplier_16b/p		67993165784896	0		281462092005375

Overflow Handling

Heading II

Heading III

Heading IV.

Heading V.


End Flag Generator

To generate a valid *end_flag* signal for the ALU, a Timed Mealy State Machine is introduced into the circuit. For pipelining circuit, the *end_flag* will result in the output after counting 4 synchronized clock cycles when the “load” signal goes from high to low. The counting of the clock cycle is implemented by rotating a vector signal to avoid introducing extra addition circuit. For non-pipelining circuit, the *end_flag* will result in the output a clock later after the “load” signal goes from high to low.

The ASMD charts are presented in Figure 30.

Figure 30

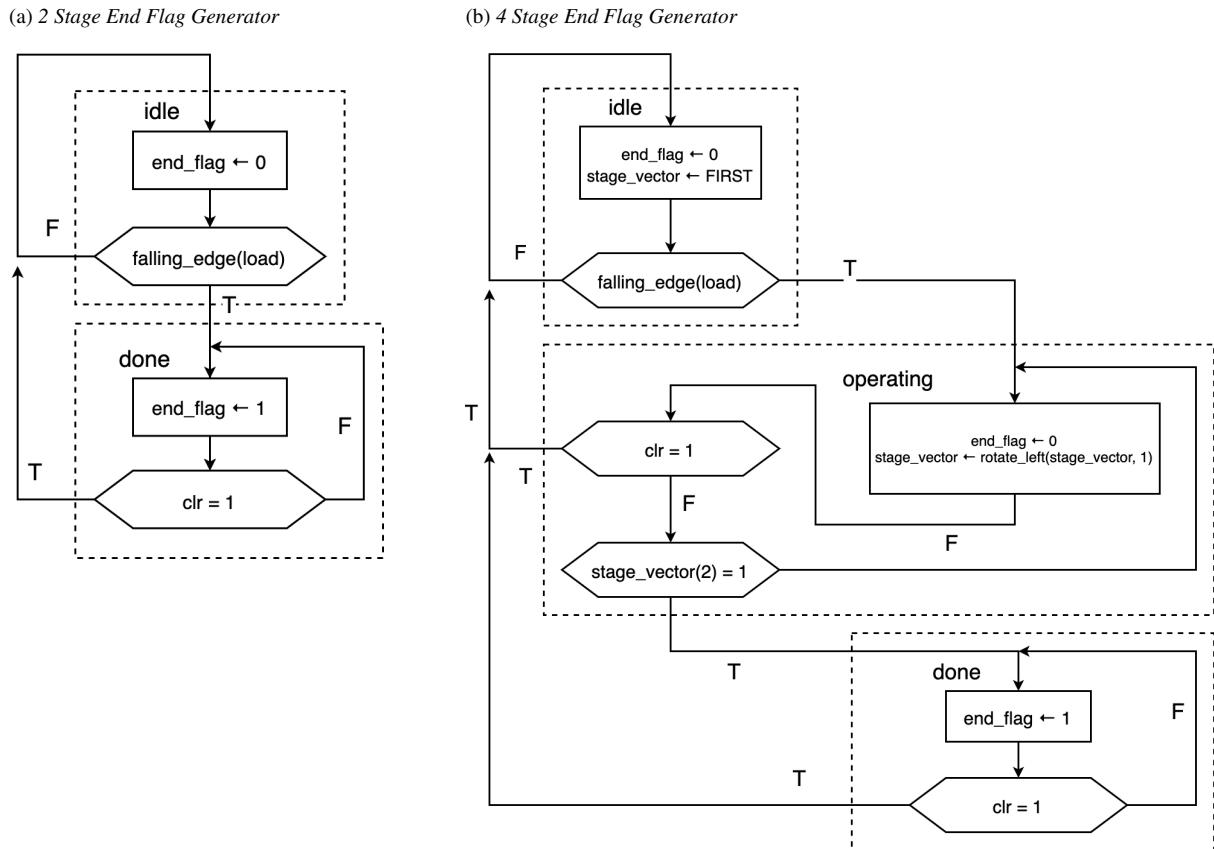ASMD Chart of the FSM of Different End Flag Generator



Note. In (b), the “stege_vector” is a 3 bit vector signal and the “FIRST” is “001”.

Non-pipelining Implementation

Heading II

Heading III

Heading IV.

Heading V.

Pipelining Implementation

Heading II

Heading III

Heading IV.

Heading V.

Synthesis and Analysis of the Arithmetic Circuit

Heading II

Heading III

Heading IV.

Heading V.

References

Cervantes Saavedra, M. d., Raffel, B., & Wilson, D. d. A. (1999). *Don Quijote: a new translation, backgrounds and contexts, criticism* (1st ed ed.). New York: W.W. Norton.

Figure 31

Synthesized RTL Diagram of 16-bit Radix-4 Booth Multiplier

